



Tanta University

**Electrical Power and Machines Engineering Department**



Faculty of Engineering

---

# ELECTRICAL POWER SYSTEM (1)

## EXPERIMENTS

### FOR 2<sup>ND</sup> YEAR STUDENT

### 2017

Eng. Eman Gaber

Eng. Mohamed Elkadeem


Eng. Mahmoud Elkazaz

Eng. Abd El-Aziz Gebril

# CONTENTS


---

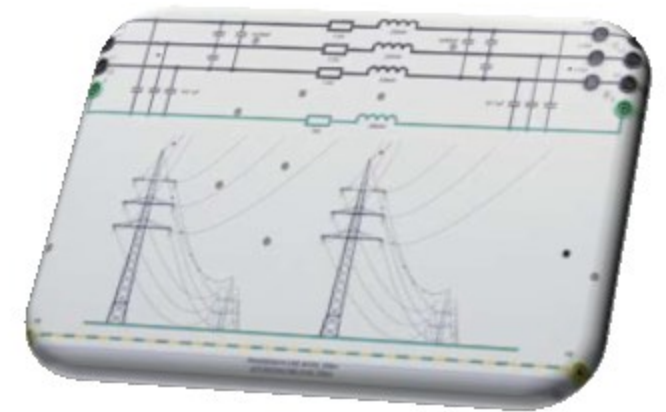1. Performance of short transmission lines
2. Determination of short transmission line model constants
3. Performance of Medium Transmission Lines ( $\pi$ -Model)
- 4. Performance of Medium Transmission Lines (T-Model)**
5. Determination of the Dc Distributor Performance
6. Potential Distribution Over a String of Suspension Insulators



# OUTLINES

---

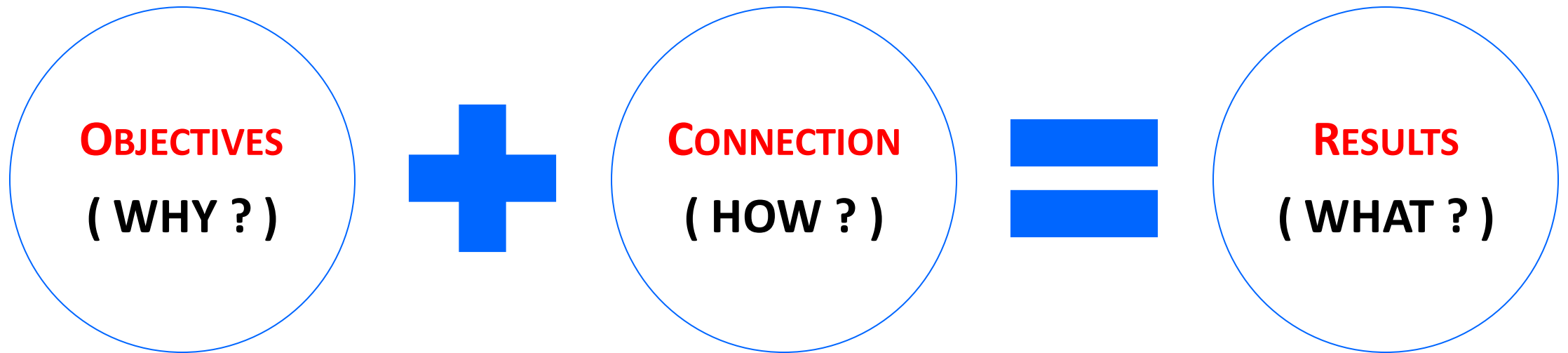

# EXP (1)

---

## Performance of Medium Transmission Lines ( T-Model )

**80 km < L < 250 km + Up to 100 kV**


# OBJECTIVES

TL resistance ( $R_{av}$ ), reactance ( $X_{av}$ )  
and substance ( $Y_{av}$ )


C/Cs of the medium TL

Plot the phasor diagram at lag, unity, and lead power factors

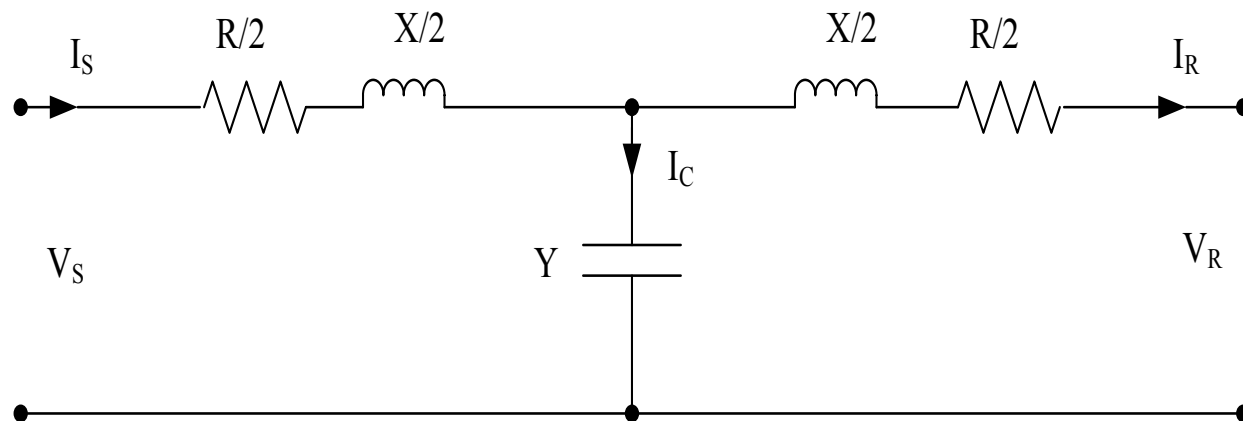**Medium TL**  
**(from 80 up to 250 km)**




# CONNECTION DIAGRAM

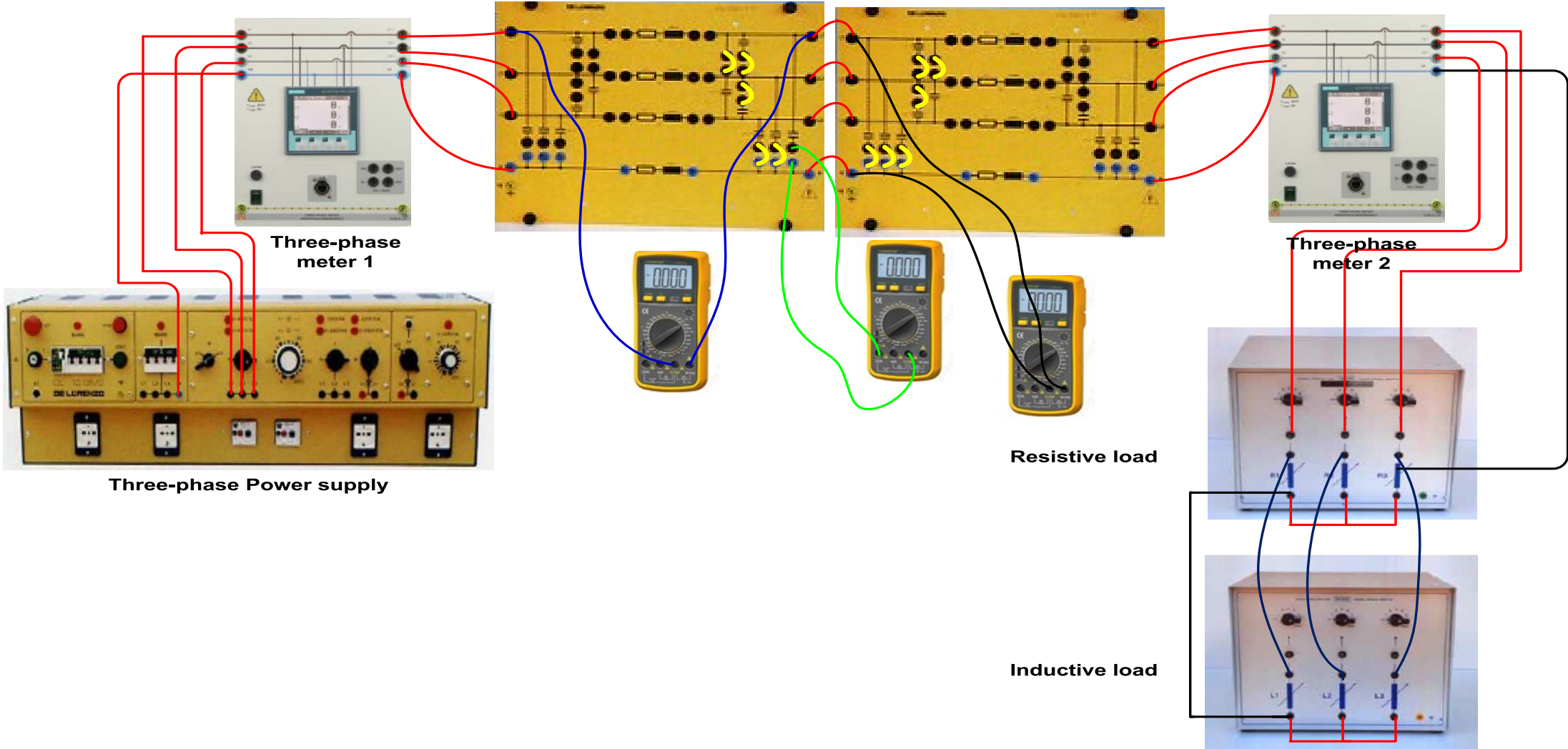

# RESULTS




| R | V <sub>s</sub> | I <sub>r</sub> | V <sub>r</sub> | P <sub>r</sub> | P <sub>s</sub> | V <sub>c</sub> | I <sub>c</sub> | I <sub>L</sub> | ΔV/2 | ζ% | ε% | R | Z | Y | X <sub>L</sub> |
|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|------|----|----|---|---|---|----------------|
| ∞ | ✓              | ✓              | ✓              | ✓              | ✓              | ✓              | ✓              | ✓              | ✓    | ?  | ?  | ? | ? | ? | ?              |
| 1 |                |                |                |                |                |                |                |                |      |    |    |   |   |   |                |
| 2 |                |                |                |                |                |                |                |                |      |    |    |   |   |   |                |
| 3 |                |                |                |                |                |                |                |                |      |    |    |   |   |   |                |
| 4 |                |                |                |                |                |                |                |                |      |    |    |   |   |   |                |
| 5 |                |                |                |                |                |                |                |                |      |    |    |   |   |   |                |

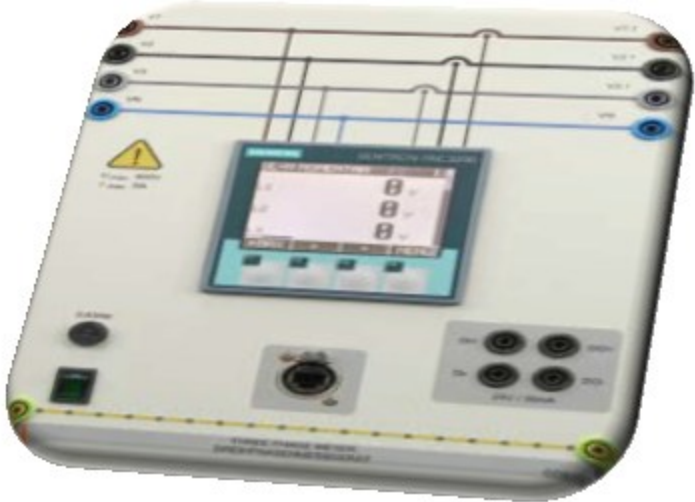


**R<sub>av</sub>, X<sub>av</sub> & Y<sub>av</sub> ???**

# RESULTS

---

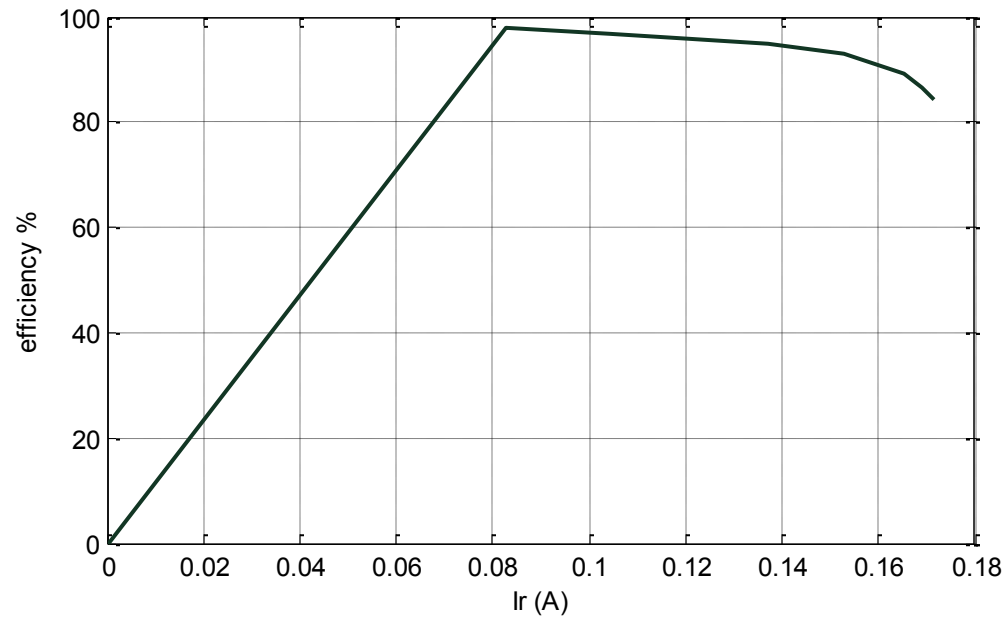


Efficiency % and load current (T-model)

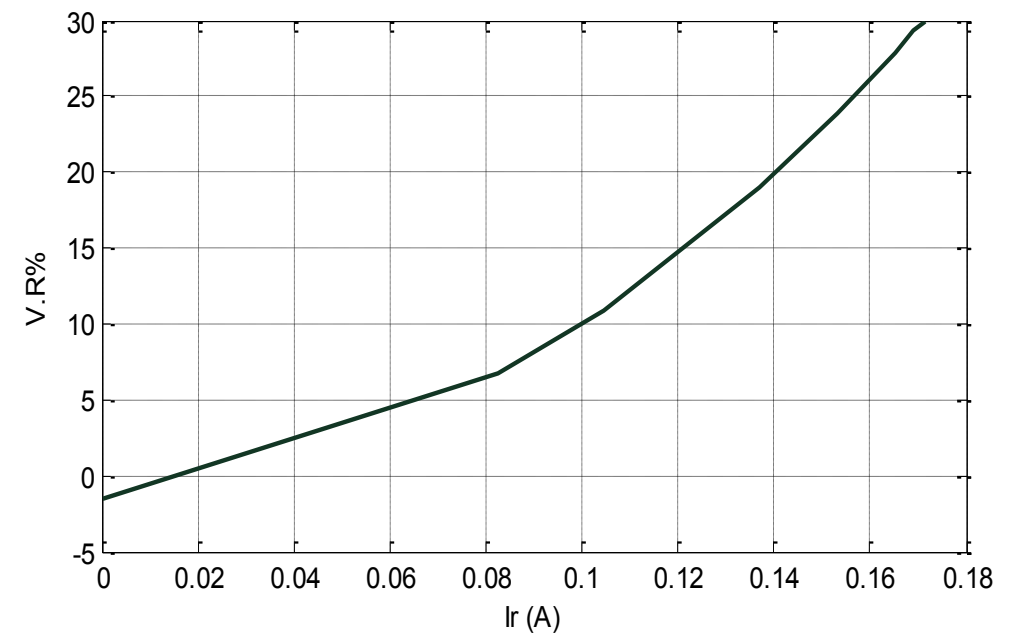


Voltage regulation % and load current (T-model)




# RESULTS

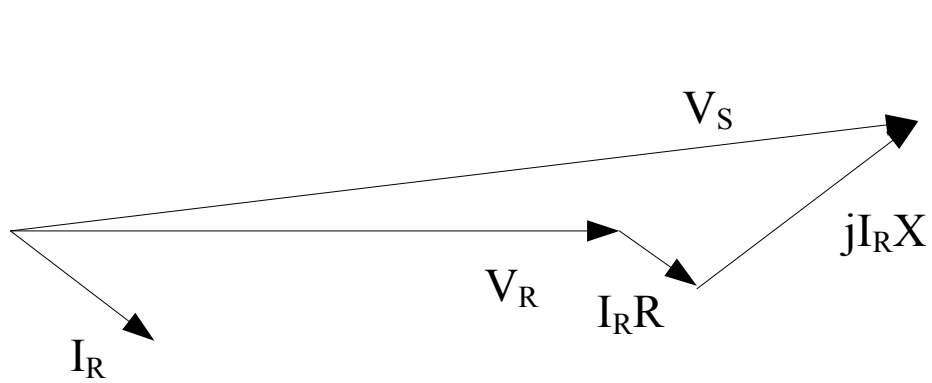

Phasor diagram with **Lagging PF**

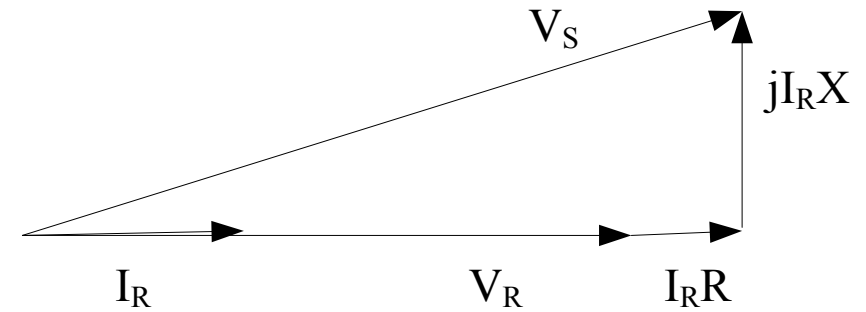

**Unity PF**

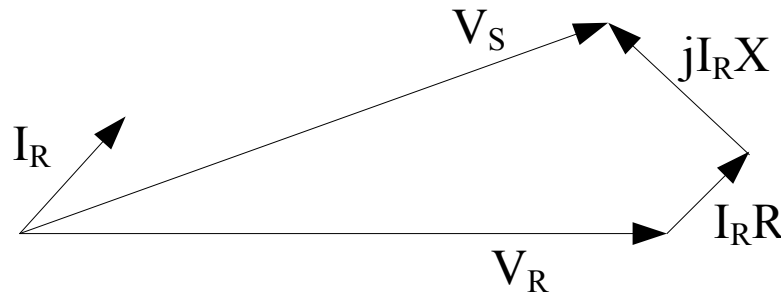

**Leading PF**

# QUESTIONS

---

1. Plot the phasor diagram at one recording data.
2. Calculate average TL resistance, inductance and capacitance.
3. Repeat these steps at unity power factor.
4. Repeat these steps at lead power factor.
5. Draw the efficiency and voltage regulation against IR for lag, lead and unity power factor on one figure.
6. Write your comment for all results.

# DISCUSSION

---

1. What is the effect of load power factor on voltage regulation and efficiency of medium transmission lines?
2. A medium transmission line is open circuited at the receiving end. Will there be any current in the line at the sending end? Explain your answer

# RESULTS

---

WHAT DO THE MEASUREMENT RESULTS INDICATE ? !

Comments !!



# EXP.4 RESULTS

| R   | $V_s$<br>v | $I_s$<br>mA | $I_r$<br>mA | $V_r$<br>v | $P_s$<br>w | $P_r$<br>w | $I_c$<br>mA | $\Delta V/2$<br>v | $V_c$<br>v | $pf_s$ | $pf_r$ |
|-----|------------|-------------|-------------|------------|------------|------------|-------------|-------------------|------------|--------|--------|
| O.C | 85         | -           | 0           | 80         | -          | 0          | -           | -                 | -          | -      | -      |
| 1   | 100        | 80          | 170         | 80         | 10         | 8          | 60          | 7                 | 96         | 0.93   | 0.56   |
| 2   | 105        | 150         | 230         | 80         | 17         | 14         | 63          | 14                | 101        | 0.96   | 0.78   |
| 3   | 113        | 240         | 290         | 80         | 23         | 20         | 66          | 21                | 106        | 0.9    | 0.87   |
| 4   | 120        | 290         | 360         | 80         | 31         | 27         | 69          | 30                | 110        | 0.88   | 0.92   |
| 5   | 130        | 360         | 440         | 80         | 37         | 33         | 71          | 33                | 113        | 0.85   | 0.95   |

# EXP.4 RESULTS

---

جدول النتائج  
كامل  
ورق A4

الرسومات  
( ورق رسم بياني  
+ مسطرة)

إجابة الأسئلة

Comments

# THANKS